



Umwandlung von Impedanzen

GRUNDLAGEN



SCAN ME

Umwandlungen am Transformator

Tor 1	A allgemein	A reziprok	A reziprok	H allgemein	H reziprok	H reziprok
Z_1	$\frac{A_{11}}{A_{22}} Z_2$	$(A_{11})^2 Z_2$	$\frac{1}{(A_{22})^2} Z_2$	$H_{12} H_{21} Z_2$	$(H_{12})^2 Z_2$	$(H_{21})^2 Z_2$
C_1	$\frac{A_{22}}{A_{11}} C_2$	$\frac{1}{(A_{11})^2} C_2$	$(A_{22})^2 C_2$	$\frac{1}{H_{12} H_{21}} C_2$	$\frac{1}{(H_{12})^2} C_2$	$\frac{1}{(H_{21})^2} C_2$
L_1	$\frac{A_{11}}{A_{22}} L_2$	$(A_{11})^2 L_2$	$\frac{1}{(A_{22})^2} L_2$	$H_{12} H_{21} L_2$	$(H_{12})^2 L_2$	$(H_{21})^2 L_2$
Y_1	$A_{11} Y_2$	$A_{11} Y_2$	$A_{11} Y_2$	$H_{12} Y_2$	$H_{12} Y_2$	$H_{12} Y_2$
I_{X1}	$-A_{22} I_{X2}$	$-A_{22} I_{X2}$	$-A_{22} I_{X2}$	$\frac{1}{H_{21}} I_{X2}$	$\frac{1}{H_{21}} I_{X2}$	$\frac{1}{H_{21}} I_{X2}$

Umwandlungen am Gyrator

Tor 1	A allgemein	A reziprok	A reziprok	Y allgemein	Y reziprok	Y reziprok
Z_1	$\frac{A_{12}}{A_{21}} \frac{1}{Z_2}$	$(A_{12})^2 \frac{1}{Z_2}$	$\frac{1}{(A_{21})^2} \frac{1}{Z_2}$	$\frac{1}{G_{12} G_{21}} \frac{1}{Z_2}$	$\frac{1}{(G_{12})^2} \frac{1}{Z_2}$	$\frac{1}{(G_{21})^2} \frac{1}{Z_2}$
C_1	$\frac{A_{21}}{A_{12}} L_2$	$\frac{1}{(A_{12})^2} L_2$	$(A_{21})^2 L_2$	$G_{12} G_{21} L_2$	$(G_{12})^2 L_2$	$(G_{21})^2 L_2$
L_1	$\frac{A_{12}}{A_{21}} C_2$	$(A_{12})^2 C_2$	$\frac{1}{(A_{21})^2} C_2$	$\frac{1}{G_{12} G_{21}} C_2$	$\frac{1}{(G_{12})^2} C_2$	$\frac{1}{(G_{21})^2} C_2$
Y_1	$-A_{12} I_{X2}$	$-A_{12} I_{X2}$	$-A_{12} I_{X2}$	$\frac{1}{G_{21}} I_{X2}$	$\frac{1}{G_{21}} I_{X2}$	$\frac{1}{G_{21}} I_{X2}$
I_{X1}	$A_{21} Y_2$	$A_{21} Y_2$	$A_{21} Y_2$	$G_{12} Y_2$	$G_{12} Y_2$	$G_{12} Y_2$